

Modeling and Implementation of Wave Digital Filters

Sound Analysis, Synthesis and Processing
Module 2 - Sound Synthesis and Spatial Processing

Oliviero Massi, Alberto Bernardini, Davide Albertini

M.Sci. on Music and Acoustic Engineering
Politecnico di Milano

May 9, 2025

Introduction

Definition of Wave Variables

Modeling the Elements

Modeling the Topology

Connection Tree Structures

Example of Application

Introduction

Definition of Wave Variables

Modeling the Elements

Modeling the Topology

Connection Tree Structures

Example of Application

- In its long history and evolution, **Circuit Theory** has had a formidable impact in nearly all fields of engineering
- Various lumped linear and nonlinear systems can be represented using **equivalent electrical networks**
- The model of an electrical circuit is made of
 - Equations describing the **network topology** called:
 - *Kirchhoff Voltage Laws* (KVL)
 - *Kirchhoff Current Laws* (KCL)
 - Constitutive equations of **circuit elements** such as:
 - *One-port elements* (e.g., sources, resistors, capacitors, inductors, diodes)
 - *Multi-port elements* (e.g., opamps, transformers, gyrators, transistors, vacuum tubes)

- Kirchhoff descriptions of circuits are characterized by **multivariate systems of Ordinary Differential Equations (ODEs)**
- In order to numerically simulate a circuit, suitable **discretization methods** are needed for approximating time derivatives in the discrete-time domain
- **Computability problem:** when implicit discretization methods are used, **the resulting system of discrete-time equations is implicit**
 - Constitutive equations and topological information are merged

- **Widely Adopted Solution:** using multivariate iterative solvers, such as Newton-Raphson solvers, whose dimensionality roughly equals the number of nodes (or loops) in the circuit
- Such a solution is *adopted in all the mainstream simulation methods* formulated in the Kirchhoff domain, such as:
 - Modified Nodal Analysis (MNA) method (SPICE-like software)
 - Sparse-Tableau method
 - State-Space methods
 - Port-Hamiltonian methods

- Wave Digital Filter (WDF) theory developed by A. Fettweis during the 70s was *originally conceived as a methodology for modeling digital filters by discretizing reference analog circuits*
- WDF theory poses the basis for completely *new methods for emulating linear and nonlinear circuits* in the Wave Digital (WD) domain



Figure: Photo of Alfred Fettweis.

- A WDF is derived discretizing a *reference analog circuit*
- Circuit elements and circuit topology are modeled separately
- One-port circuit elements are modeled as *input-output blocks* characterized by scattering relations
- Topological interconnections of elements are modeled using multi-input-multi-output *junctions* characterized by scattering matrices
- Elements and junctions are modeled in a *port-wise fashion*
- Each port of an element or junction is characterized by a pair of port variables called *wave variables*
- One introduced *free parameter* per port

Introduction

Definition of Wave Variables

Modeling the Elements

Modeling the Topology

Connection Tree Structures

Example of Application

Definition of Voltage Waves

- **Kirchhoff variables** at port n (of a generic port element or junction) are
 - the port voltage v_n
 - the port current i_n
- **Wave variables** (voltage waves) are defined as [1]

$$a_n = v_n + Z_n i_n \quad b_n = v_n - Z_n i_n \quad (1)$$

- a_n is the incident wave
 - b_n is the reflected wave
 - $Z_n \neq 0$ is a scalar free parameter called *reference port resistance*
- Inverse mapping

$$v_n = \frac{a_n + b_n}{2} \quad i_n = \frac{a_n - b_n}{2Z_n} \quad (2)$$

- Kirchhoff-to-Wave linear transformation

$$\begin{bmatrix} a_n \\ b_n \end{bmatrix} = \begin{bmatrix} 1 & Z_n \\ 1 & -Z_n \end{bmatrix} \begin{bmatrix} v_n \\ i_n \end{bmatrix} \quad (3)$$

- Wave-to-Kirchhoff linear transformation

$$\begin{bmatrix} v_n \\ i_n \end{bmatrix} = \frac{1}{2} \begin{bmatrix} 1 & 1 \\ 1/Z_n & -1/Z_n \end{bmatrix} \begin{bmatrix} a_n \\ b_n \end{bmatrix} \quad (4)$$

Introduction

Definition of Wave Variables

Modeling the Elements

Modeling the Topology

Connection Tree Structures

Example of Application

Constitutive Equations of One-Port Elements

- In the **continuous-time domain** (t is the time variable)

$$h(v(t), i(t)) = 0 \quad (5)$$

- $v(t)$ is the port voltage and $i(t)$ is the port current
 - h is a (linear or nonlinear) dynamic or instantaneous function
- In the **discrete-time domain**

$$\tilde{h}(v[k], i[k]) = 0 \quad (6)$$

- $v[k] = v(kT_s)$ and $i[k] = i(kT_s)$, where k is the sampling index and $F_s = 1/T_s$ is the sampling frequency
 - if the element is memoryless we have that $\tilde{h}(x, y) = h(x, y)$, otherwise $\tilde{h}(x, y) \neq h(x, y)$

- The majority of linear one-port elements **in the discrete-time domain** is characterized by a *constitutive equation* in the form

$$v[k] = R_e[k]i[k] + V_e[k] \quad (7)$$

- $R_e[k]$ is a resistance parameter
- $V_e[k]$ is a voltage bias parameter

- In the continuous-time domain the *constitutive equation* of a linear resistor with resistance R is

$$v(t) = Ri(t) \quad (8)$$

- In the discrete-time domain we get

$$v[k] = Ri[k] \quad (9)$$

- Eq. (9) is a special case of eq. (7) in which:
 - $R_e[k] = R$
 - $V_e[k] = 0$

- In the continuous-time domain the *constitutive equation* of a linear resistive voltage source with source signal $V_g(t)$ and internal series resistance R_g is

$$v(t) = R_g i(t) + V_g(t) \quad (10)$$

- In the discrete-time domain we get

$$v[k] = R_g i[k] + V_g[k] \quad (11)$$

- Eq. (11) is a special case of eq. (7) in which:
 - $R_e[k] = R_g$
 - $V_e[k] = V_g[k] = V_g(kT_s)$

- In the **continuous-time domain** the *constitutive equation* of a linear dynamic element (capacitor or inductor) is

$$y(t) = \mu \frac{dx(t)}{dt} \quad (12)$$

- $x(t)$ is a port voltage or port current
- $y(t)$ is a port current or port voltage
- μ is a (capacitive or inductive) real coefficient
- In the **Laplace domain**, where s is the complex frequency variable, (12) is written as

$$Y(s) = s\mu X(s) \quad (13)$$

Mappings from the Laplace domain with complex frequency variable s to the Z-domain with complex variable $z = e^{sT_s}$

- **Backward Euler Method**

$$s \leftarrow \frac{1 - z^{-1}}{T_s} \quad (14)$$

- **Trapezoidal Rule** (a.k.a. bilinear transform or Tustin's method)

$$s \leftarrow \frac{2}{T_s} \frac{1 - z^{-1}}{1 + z^{-1}} \quad (15)$$

- Many other discretization methods are usable (e.g., finite difference methods, Runge-Kutta methods, etc. ...)

- According to (15), *frequencies referred to the discrete-time domain* are mapped to *frequencies referred to the continuous-time domain* by the substitution

$$j\omega \leftarrow \frac{2}{T_s} \frac{e^{j\tilde{\omega}T_s} - 1}{e^{j\tilde{\omega}T_s} + 1} \quad (16)$$

where ω satisfies $s = j\omega$ and $\tilde{\omega}$ satisfies $z = e^{j\tilde{\omega}T_s}$

- After some simplifications (16) can be rewritten as

$$j\omega \leftarrow j \frac{2}{T_s} \tan \left(\tilde{\omega} \frac{T_s}{2} \right) \quad (17)$$

- According to (17), it is possible to express in closed-form the reference “continuous-time frequency” ω as a function of the “discrete-time frequency” $\tilde{\omega}$ using the **warping mapping**

$$\omega = \frac{2}{T_s} \tan \left(\tilde{\omega} \frac{T_s}{2} \right) \quad (18)$$

- ω is really close to $\tilde{\omega}$ at low frequencies, while they differ more and more at high frequencies
- The higher the sampling frequency $F_s = 1/T_s$, the more the difference between ω and $\tilde{\omega}$ becomes negligible in the whole frequency range of interest

- In the Laplace domain the *constitutive equation* of a linear capacitor with capacitance C is

$$I(s) = sCV(s) \quad (19)$$

- After applying the bilinear transform (15) to (19), in the discrete-time domain we get

$$v[k] = \frac{T_s}{2C}i[k] + \frac{T_s}{2C}i[k-1] + v[k-1] \quad (20)$$

- Eq. (20) is a special case of eq. (7) in which [2]:
 - $R_e[k] = T_s/(2C)$
 - $V_e[k] = T_si[k-1]/(2C) + v[k-1]$

- In the Laplace domain the *constitutive equation* of a linear inductor with inductance L is

$$V(s) = sLI(s) \quad (21)$$

- After applying the bilinear transform (15) to (21), in the discrete-time domain we get

$$v[k] = \frac{2L}{T_s}i[k] - \frac{2L}{T_s}i[k-1] - v[k-1] \quad (22)$$

- Eq. (22) is a special case of eq. (7) in which [2]:
 - $R_e[k] = 2L/T_s$
 - $V_e[k] = -(2Li[k-1])/T_s - v[k-1]$

- Wave-to-Kirchhoff transformation in the discrete-time domain

$$v[k] = \frac{a[k] + b[k]}{2} \quad , \quad i[k] = \frac{a[k] - b[k]}{2Z[k]} \quad (23)$$


- Applying the substitution (23) in (7) and solving for $b[k]$, we get the **scattering relation** of a generic linear one-port element

$$b[k] = \frac{R_e[k] - Z[k]}{R_e[k] + Z[k]} a[k] + \frac{2Z[k]}{R_e[k] + Z[k]} V_e[k] \quad (24)$$


- Adaptation case** (the instantaneous dependency of $b[k]$ from $a[k]$ is eliminated)

$$b[k] = V_e[k] \quad , \quad \text{with} \quad Z[k] = R_e[k] \quad (25)$$
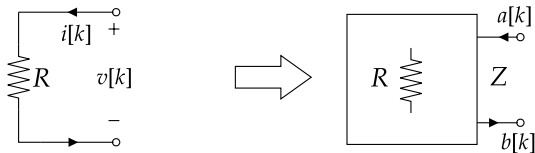
$$b[k] = V_e[k] = 0, \quad \text{Adaptation: } Z = R_e[k] = R$$




ADAPTATION

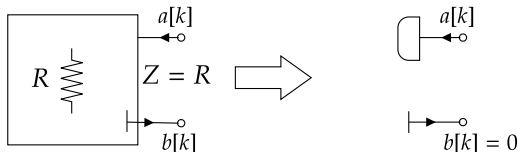


WD Resistive Voltage Source

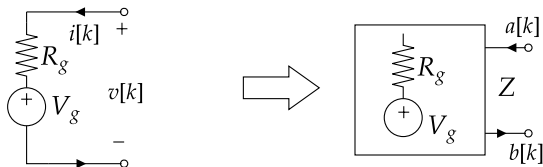
$$b[k] = V_e[k] = V_g[k], \quad \text{Adaptation: } Z = R_e[k] = R_g$$




ADAPTATION

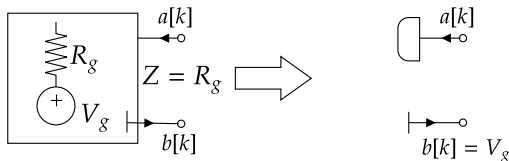

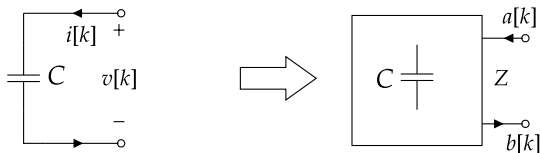
$$b[k] = V_e[k] = \frac{T_s}{2C} i[k-1] + v[k-1], \quad \text{Adaptation: } Z = R_e[k] = \frac{T_s}{2C}$$



ADAPTATION

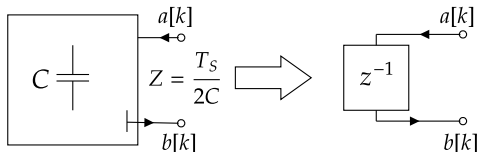
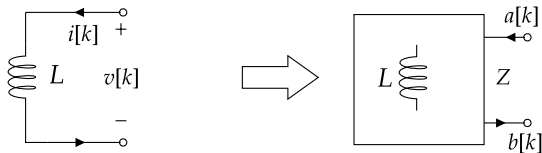
$$b[k] = V_e[k] = -\frac{2L}{T_s}i[k-1] - v[k-1], \quad \text{Adaptation: } Z = R_e[k] = \frac{2L}{T_s}$$



ADAPTATION

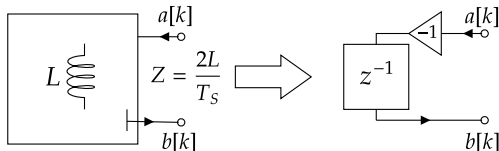


Table: *Wave mappings of common WD linear one-port elements.*

Constitutive Eq.	Wave Mapping	Adaptation Condition
$v(t) = V_g(t) + R_g i(t)$	$b[k] = V_g[k]$	$Z[k] = R_g$
$v(t) = Ri(t)$	$b[k] = 0$	$Z[k] = R$
$i(t) = C \frac{dv(t)}{dt}$	$b[k] = a[k - 1]$	$Z[k] = \frac{T_s}{2C}$
$v(t) = L \frac{di(t)}{dt}$	$b[k] = -a[k - 1]$	$Z[k] = \frac{2L}{T_s}$

- Shockley diode model for exponential p–n junction diodes

$$i(t) = I_s \left(e^{v(t)/(\eta V_{th})} - 1 \right) \quad (26)$$

- saturation current I_s
- thermal voltage V_{th}
- ideality factor η
- Eq. (26) is nonlinear and it cannot be put in the form (7)

- Substitute (23) into the discrete-time version of eq. (26)
- The result is a *transcendental equation* in the WD domain
- The following closed-form solution for $b[k]$ can be found [3, 4]

$$b[k] = a[k] + 2Z[k]I_s - 2\eta V_{th} W \left(\frac{Z[k]I_s}{\eta V_{th}} e^{\frac{Z[k]I_s + a[k]}{\eta V_{th}}} \right) \quad (27)$$

- $W(x)$ is the *Lambert Function* implicitly defined as

$$x = W(x)e^{W(x)}$$

- The nonlinear WD diode cannot be adapted!

Introduction

Definition of Wave Variables


Modeling the Elements

Modeling the Topology


Connection Tree Structures

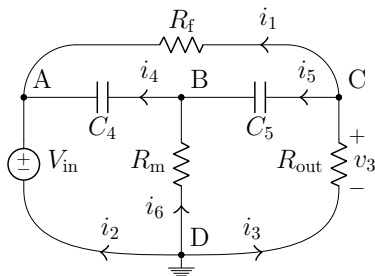Example of Application

- A N -port topological junction is an open interconnection network (i.e., without *electrical loads*) characterized by
 - a vector of port voltages $\mathbf{v} = [v_1, \dots, v_N]^T$
 - a vector of port currents $\mathbf{i} = [i_1, \dots, i_N]^T$
- Example:



(a) Reference circuit.

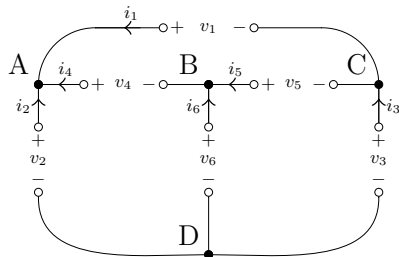

(b) Topological connection network.

- Found a *subset of independent port voltages* we have that

$$\mathbf{v} = \mathbf{Q}^T \mathbf{v}_t \quad (28)$$

- \mathbf{v}_t is the vector of size $q \times 1$ collecting independent port voltages
- \mathbf{Q} is the **fundamental cut-set matrix** of size $q \times N$
- Found a *subset of independent port currents* we have that

$$\mathbf{i} = \mathbf{B}^T \mathbf{i}_l \quad (29)$$



- \mathbf{i}_l is the vector of size $p \times 1$ collecting independent port currents
- \mathbf{B} is the **fundamental loop matrix** of size $p \times N$
- $p + q = N$
- Orthogonality property

$$\mathbf{B}\mathbf{Q}^T = \mathbf{0}_{p \times q} \quad , \quad \mathbf{Q}\mathbf{B}^T = \mathbf{0}_{q \times p} \quad (30)$$

How to find independent port variables?



- Consider the **digraph \mathcal{D} of the reference circuit** where the *edges* represent the loads of the connection network (one per port), while the *vertices* represent the nodes of the circuit [5]
- Apply a **tree-cotree decomposition** to \mathcal{D}
 - A **tree \mathcal{T}** of \mathcal{D} is defined as *a connected acyclic subgraph of \mathcal{D} containing all vertices*
 - A **cotree \mathcal{C}** of \mathcal{D} is *a subgraph of \mathcal{D} containing all the edges of \mathcal{D} that are not in a reference tree \mathcal{T}*
- **Independent port voltages** in \mathbf{v}_t are those *related to the edges of the tree*
- **Independent port currents** in \mathbf{i}_l are those *related to the edges of the cotree*

Example 1: Series Connection Network

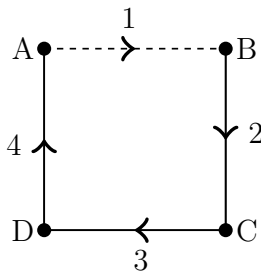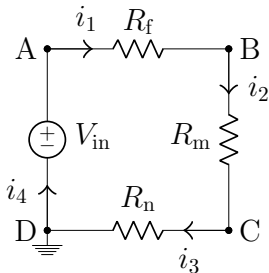



$$\mathbf{i} = \mathbf{B}^T \mathbf{i}_l \quad \rightarrow \quad \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \\ 1 \\ 1 \end{bmatrix} i_1 \quad (31)$$

Example 2: Parallel Connection Network

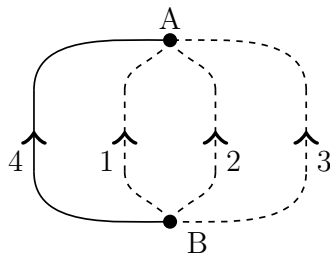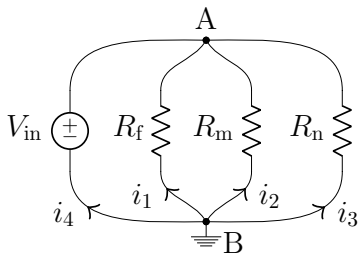

$$\mathbf{v} = \mathbf{Q}^T \mathbf{v}_t \rightarrow \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \\ 1 \\ 1 \end{bmatrix} v_4 \quad (32)$$

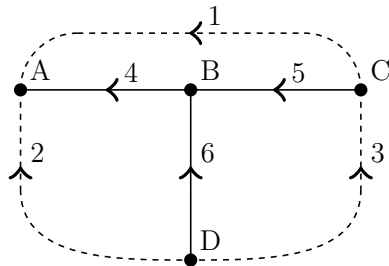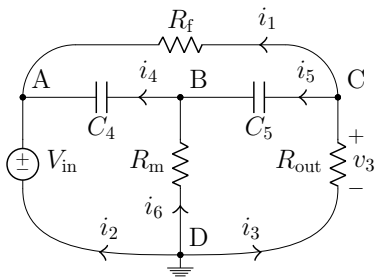Example 3: Bridged-Tee Connection Network



$$\mathbf{i} = \mathbf{B}^T \mathbf{i}_l \rightarrow \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & -1 & 0 \\ -1 & 0 & 1 \\ 0 & -1 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} \quad (33)$$

WD Junctions (Adaptors)

- In the WD domain a topological connection network is modeled as a **WD scattering junction** (also called *adaptor*)
- Kirchhoff-to-Wave mapping of port variables

$$\mathbf{a} = \mathbf{v} + \mathbf{Z}\mathbf{i} \quad , \quad \mathbf{b} = \mathbf{v} - \mathbf{Z}\mathbf{i} \quad (34)$$

- $\mathbf{a} = [a_1, \dots, a_N]^T$ vector of waves incident to the junction
- $\mathbf{b} = [b_1, \dots, b_N]^T$ vector of waves reflected by the junction
- $\mathbf{Z} = \text{diag}[Z_1, \dots, Z_N]$ is the diagonal matrix of free parameters
- Scattering relation

$$\mathbf{b} = \mathbf{S}\mathbf{a} \quad (35)$$

- \mathbf{S} is a $N \times N$ scattering matrix

- If $q \leq p$ use

$$\mathbf{S} = 2\mathbf{Q}^T(\mathbf{Q}\mathbf{Z}^{-1}\mathbf{Q}^T)^{-1}\mathbf{Q}\mathbf{Z}^{-1} - \mathbf{I} \quad (36)$$

- \mathbf{I} is the $N \times N$ identity matrix
- the inversion of the $q \times q$ matrix $\mathbf{Q}\mathbf{Z}^{-1}\mathbf{Q}^T$ is required
- If $q \geq p$

$$\mathbf{S} = \mathbf{I} - 2\mathbf{Z}\mathbf{B}^T(\mathbf{B}\mathbf{Z}\mathbf{B}^T)^{-1}\mathbf{B} \quad (37)$$

- \mathbf{I} is the $N \times N$ identity matrix
- the inversion of the $p \times p$ matrix $\mathbf{B}\mathbf{Z}\mathbf{B}^T$ is required

- One port of a topological WD junction can be made **reflection-free** (we say *the port is adapted*)
- The n th port of a WD junction is made reflection-free if the n th diagonal entry s_{nn} of \mathbf{S} is imposed to be zero

$$s_{nn} = 0 \quad (38)$$

- Condition (38) can be satisfied by properly setting the free parameter Z_n
- Examples
 - The n th port of a N -port series WD junction is made reflection-free by setting $Z_n = \sum_{k \neq n} Z_k$
 - The n th port of a N -port parallel WD junction is made reflection-free by setting $Z_n^{-1} = \sum_{k \neq n} Z_k^{-1}$

Introduction

Definition of Wave Variables

Modeling the Elements


Modeling the Topology


Connection Tree Structures

Example of Application

- The WDF is modeled as a **connection tree**
- *The nonlinear one-port element* is the **root**
- *WD topological junctions* are the **nodes**
 - *Ports of WD junctions either connected to other WD junctions or to the nonlinear element are made reflection-free*
- *Linear WD one-port elements* are the **leaves**
 - *Linear WD elements are all adapted*
- In case the topology is solely made of *series-parallel connections*, the WDF can be modeled as a **Binary Connection Tree (BCT)**
 - In a BCT nodes are 3-port series or parallel WD junctions [6]

Generic Connection Tree with One Node


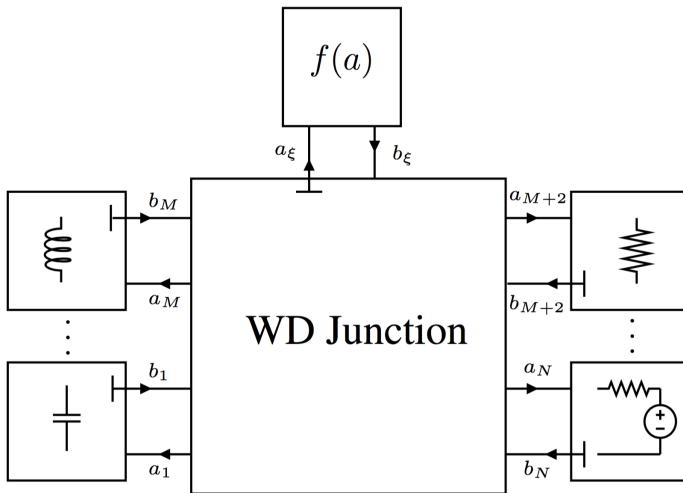


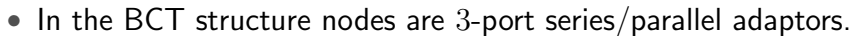

The following process is repeated at each sampling step.

- **Forward scan** from the leaves to the root
 - waves reflected by the linear elements (incident to the junctions) are computed
 - waves are propagated through the junctions up to the nonlinear element
- **Local nonlinear scattering stage** at the root
 - given the incident wave, the wave reflected by the nonlinear element is computed
- **Backward scan** from the root to the leaves
 - waves are propagated through the junctions up to the linear elements
 - waves incident to the linear elements are computed

Illustration of Computational Flow in a BCT

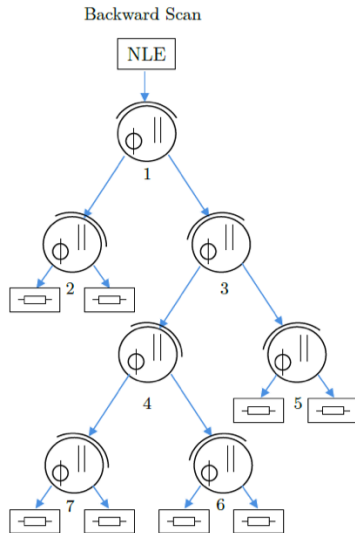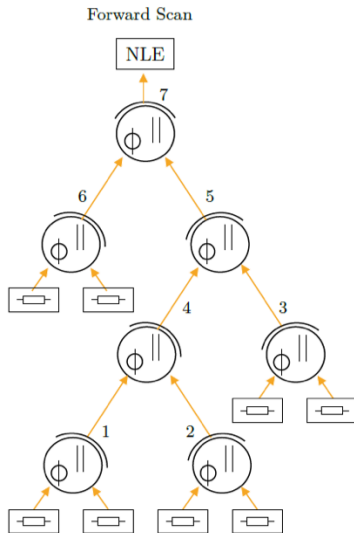

Introduction

Definition of Wave Variables

Modeling the Elements


Modeling the Topology

Connection Tree Structures


Example of Application

Envelope Follower Circuit and WDF Realization

- Reference circuit

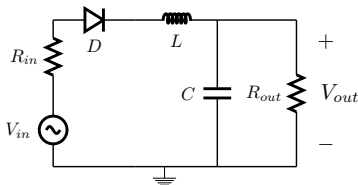

- Corresponding WDF with BCT structure

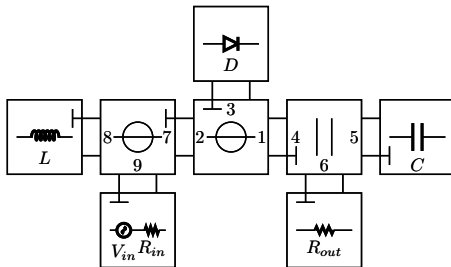

- The WDFs is composed of:
 - Four linear WD elements (input source V_{in} with series resistance R_{in} , inductor L , capacitor C and output resistance R_{out})
 - Three 3-port WD junctions (two series adaptors, one parallel adaptor)
 - One nonlinear WD element (the exponential diode D)
- Ports of 3-port adaptors are numbered;
 - the adaptor with ports number 4, number 5 and number 6 is a parallel adaptor
 - the other two are series adaptors

Examples of port connections

- The port connection between port number 1 of the series adaptor and port number 4 of the parallel adaptor on the right is performed imposing the following constraints

$$a_1[k] = b_4[k] \quad , \quad a_4[k] = b_1[k] \quad , \quad Z_1 = Z_4 \quad (39)$$

- Similarly, connection between port number 2 of the series adaptor and port number 7 of the series adaptor on the left is performed imposing the following constraints

$$a_2[k] = b_7[k] \quad , \quad a_7[k] = b_2[k] \quad , \quad Z_2 = Z_7 \quad (40)$$

- A WD block with a *T-shaped symbol* at a port is *adapted* at that port (that port is reflection-free)
- For instance, the parallel adaptor is adapted at port number 4 and all one-port WD elements are adapted, except for the diode which cannot be adapted.

- Adaptation conditions set at *ports facing linear elements* are

$$Z_9 = R_{in} \quad , \quad Z_6 = R_{out} \quad , \quad Z_5 = T_s/(2C) \quad , \quad Z_8 = (2L)/T_s \quad (41)$$

- Adaptation conditions set at *ports facing other adaptors* are

$$Z_1 = Z_4 = \frac{Z_5 Z_6}{Z_5 + Z_6} \quad , \quad Z_2 = Z_7 = Z_8 + Z_9 \quad , \quad Z_3 = Z_1 + Z_2 \quad (42)$$

Scattering Relations of the Elements

- Real voltage source V_{in} with series resistance R_{in}

$$a_9[k] = V_{in}[k] \quad (43)$$

- Resistor with resistance R_{out}

$$a_6[k] = 0 \quad (44)$$

- Capacitor with capacitance C

$$a_5[k] = b_5[k - 1] \quad (45)$$

- Inductor with inductance L

$$a_8[k] = -b_8[k - 1] \quad (46)$$

- Diode D

$$a_3[k] = b_3[k] + 2Z_3I_s - 2\eta V_{th} W \left(\frac{Z_3I_s}{\eta V_{th}} e^{(Z_3I_s + b_3[k]) / (\eta V_{th})} \right) \quad (47)$$

- Series adaptor with ports 1, 2, 3 and scattering matrix \mathbf{S}_{S1}

$$\begin{bmatrix} b_1[k] \\ b_2[k] \\ b_3[k] \end{bmatrix} = \mathbf{S}_{S1} \begin{bmatrix} a_1[k] \\ a_2[k] \\ a_3[k] \end{bmatrix} \quad (48)$$

- Series adaptor with ports 7, 8, 9 and scattering matrix \mathbf{S}_{S2}

$$\begin{bmatrix} b_7[k] \\ b_8[k] \\ b_9[k] \end{bmatrix} = \mathbf{S}_{S2} \begin{bmatrix} a_7[k] \\ a_8[k] \\ a_9[k] \end{bmatrix} \quad (49)$$

- Parallel adaptor with ports 4, 5, 6 and scattering matrix \mathbf{S}_{P1}

$$\begin{bmatrix} b_4[k] \\ b_5[k] \\ b_6[k] \end{bmatrix} = \mathbf{S}_{P1} \begin{bmatrix} a_4[k] \\ a_5[k] \\ a_6[k] \end{bmatrix} \quad (50)$$

Scattering Matrices of WD Junctions

$$\mathbf{S}_{S1} = \begin{bmatrix} s_{11} & s_{12} & s_{13} \\ s_{21} & s_{22} & s_{23} \\ s_{31} & s_{32} & s_{33} \end{bmatrix} = \begin{bmatrix} \gamma_{S1} & (\gamma_{S1} - 1) & (\gamma_{S1} - 1) \\ -\gamma_{S1} & (1 - \gamma_{S1}) & -\gamma_{S1} \\ -1 & -1 & 0 \end{bmatrix} ,$$

$$\mathbf{S}_{S2} = \begin{bmatrix} s_{77} & s_{78} & s_{79} \\ s_{87} & s_{88} & s_{89} \\ s_{97} & s_{98} & s_{99} \end{bmatrix} = \begin{bmatrix} 0 & -1 & -1 \\ -\gamma_{S2} & (1 - \gamma_{S2}) & -\gamma_{S2} \\ (\gamma_{S2} - 1) & (\gamma_{S2} - 1) & \gamma_{S2} \end{bmatrix} ,$$

where $\gamma_{S1} = Z_2/(Z_1 + Z_2)$ and $\gamma_{S2} = Z_8/(Z_8 + Z_9)$.

$$\mathbf{S}_{P1} = \begin{bmatrix} s_{44} & s_{45} & s_{46} \\ s_{54} & s_{55} & s_{56} \\ s_{64} & s_{65} & s_{66} \end{bmatrix} = \begin{bmatrix} 0 & (1 - \gamma_{P1}) & \gamma_{P1} \\ 1 & -\gamma_{P1} & \gamma_{P1} \\ 1 & (1 - \gamma_{P1}) & (\gamma_{P1} - 1) \end{bmatrix} ,$$

where $\gamma_{P1} = Z_5/(Z_5 + Z_6)$.

- compute waves reflected from *linear elements*

$$a_9[k] = V_{in}[k] , \quad (51)$$

$$a_6[k] = 0 , \quad (52)$$

$$a_5[k] = b_5[k - 1] , \quad (53)$$

$$a_8[k] = -b_8[k - 1] \quad (54)$$

- compute waves reflected from the *first layer of adaptors*

$$b_4[k] = (1 - \gamma_{P1})a_5[k] + \gamma_{P1}a_6[k] , \quad (55)$$

$$b_7[k] = -a_8[k] - a_9[k] \quad (56)$$

- compute waves reflected from the *second layer of adaptors*

$$a_1[k] = b_4[k] , \quad (57)$$

$$a_2[k] = b_7[k] , \quad (58)$$

$$b_3[k] = -a_1[k] - a_2[k] \quad (59)$$

- compute wave reflected by the nonlinear diode (root of the BCT)

$$a_3[k] = b_3[k] + 2Z_3I_s - 2\eta V_{th} W \left(\frac{Z_3I_s}{\eta V_{th}} e^{(Z_3I_s + b_3[k]) / (\eta V_{th})} \right) \quad (60)$$

- compute waves reflected from the second layer of adaptors toward linear elements

$$b_1[k] = \gamma_{S1}a_1[k] + (\gamma_{S1} - 1)a_2[k] + (\gamma_{S1} - 1)a_3[k] \quad , (61)$$

$$b_2[k] = -\gamma_{S1}a_1[k] + (1 - \gamma_{S1})a_2[k] + -\gamma_{S1}a_3[k] \quad . (62)$$

- compute waves reflected from the first layer of adaptors toward linear elements, i.e., waves incident to linear elements,

$$a_4[k] = b_1[k] \quad , \quad (63)$$

$$a_7[k] = b_2[k] \quad , \quad (64)$$


$$b_5[k] = a_4[k] - \gamma_{P1}a_5[k] + \gamma_{P1}a_6[k] \quad , \quad (65)$$

$$b_6[k] = a_4[k] + (1 - \gamma_{P1})a_5[k] + (\gamma_{P1} - 1)a_6[k] \quad , \quad (66)$$


$$b_8[k] = -\gamma_{S2}a_7[k] + (1 - \gamma_{S2})a_8[k] - \gamma_{S2}a_9[k] \quad , \quad (67)$$

$$b_9[k] = (\gamma_{S2} - 1)a_7[k] + (\gamma_{S2} - 1)a_8[k] + \gamma_{S2}a_9[k] \quad (68)$$


LTspice Implementation

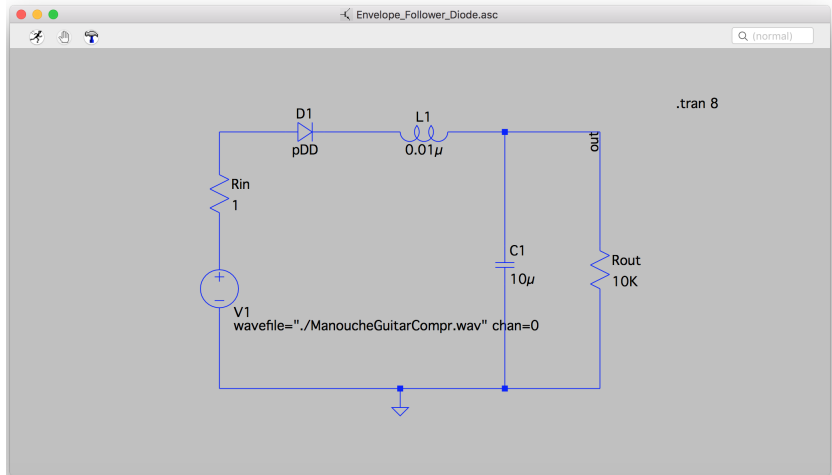

LTspice Implementation

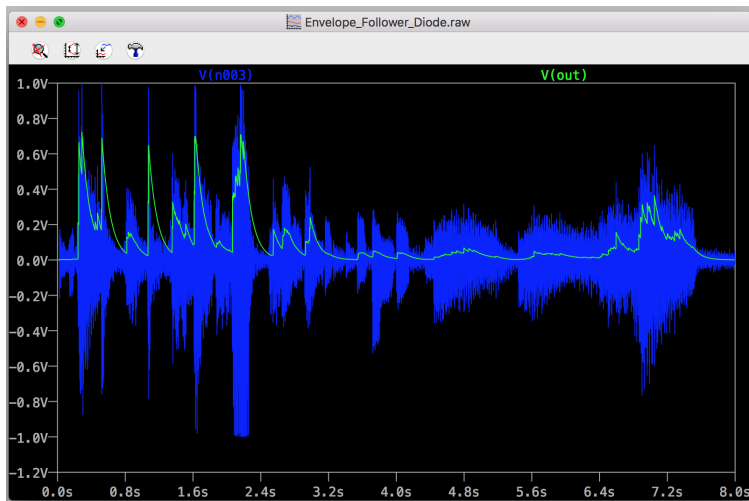

Comparison WDF vs LTspice

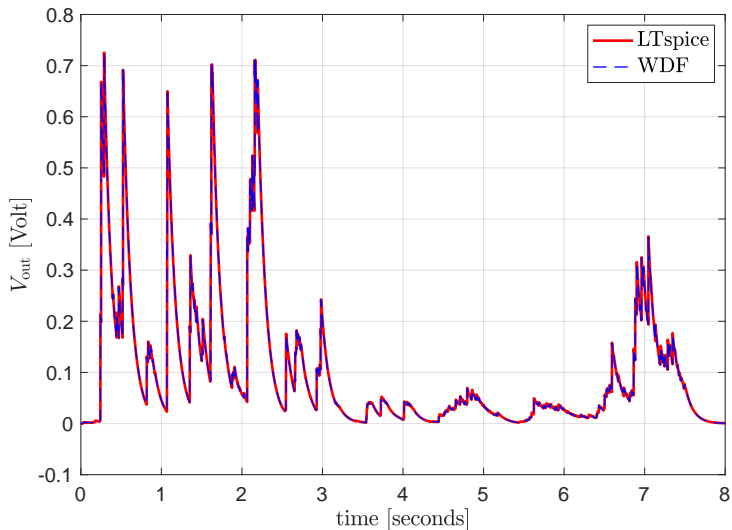

- [1] A. Fettweis. Wave digital filters: Theory and practice. *Proc. IEEE*, 74(2):270–327, Feb. 1986.
- [2] A. Bernardini, P. Maffezzoni, and A. Sarti. Linear multistep discretization methods with variable step-size in nonlinear wave digital structures for virtual analog modeling. *IEEE/ACM Transactions on Audio, Speech, and Language Processing*, 27(11):1763–1776, Nov. 2019.
- [3] R. C. De Paiva, S. D’Angelo, J. Pakarinen, and V. Välimäki. Emulation of operational amplifiers and diodes in audio distortion circuits. *IEEE Transactions on Circuits and Systems II: Express Briefs*, 59:688–692, Oct. 2012.

- [4] A. Bernardini, K. J. Werner, A. Sarti, and J. O. Smith III. Modeling nonlinear wave digital elements using the Lambert function. *IEEE Transactions on Circuits and Systems I: Regular Papers*, 63(8):1231–1242, Aug. 2016.
- [5] A. Bernardini, K. J. Werner, J. O. Smith III, and A. Sarti. Generalized wave digital filter realizations of arbitrary reciprocal connection networks. *IEEE Transactions on Circuits and Systems I: Regular Papers*, 66(2):694–707, Feb. 2019.
- [6] A. Sarti and G. De Sanctis. Systematic methods for the implementation of nonlinear wave-digital structures. *IEEE Transactions on Circuits and Systems I: Regular Papers*, 56: 460–472, Feb. 2009.

